




Analog CMOS Integrated Circuits

Exercise 10: Feedback, Stability

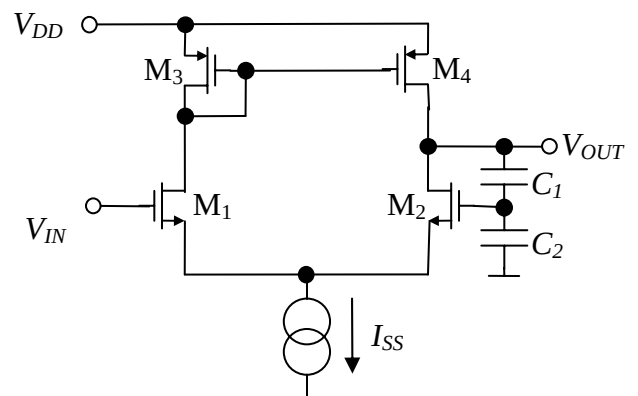
1. What feedback topology is implemented in the depicted amplifier ?

Determine the gain and output impedance at low frequency, i.e. capacitors C_1 and C_2 may not considerably load the output !



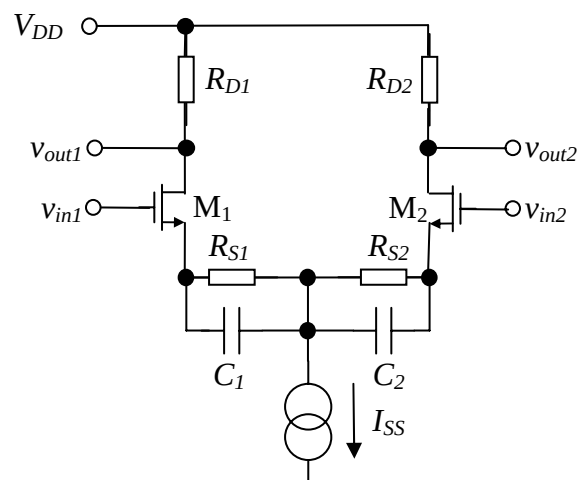2. What feedback topology is implemented in the depicted amplifier ?

Describe quantitatively the main purpose of the feedback in this circuit !



3. An amplifier may be described by a 3rd order low-pass transfer function with a DC gain of 60 dB , a double pole at 10 MHz and a third pole at 100 MHz. This amplifier has to be fed back by an RC low-pass of 1st order. The closed loop DC gain should be 20 dB. What maximum corner frequency of the feedback circuit will still enable stability of the system ?